

NAME: \_\_\_\_\_ DATE: \_\_\_\_\_



**Worksheet 11a: Introduction to Ohm's Law**

*Directions: Rely on Ohm's Law ( $V=IR$ ) to answer problems 1-16. Rely on your notes on circuits to answer the rest of the questions.*

1. The rate of electron flow is measured in (a) amperes (b) volts (c) ohms.
2. If you increase amperage and maintain resistance, do volts go up or down?
3. A \_\_\_\_\_ is the electric pressure required to produce one ampere of current in a circuit having one \_\_\_\_\_ of resistance.
4. Electric pressure is measured in \_\_\_\_\_ (\_\_\_\_): the rate of electron flow is measured in amps (\_\_\_\_), the \_\_\_\_\_ (R) is measured in ohms (\_\_\_\_).
5. In a circuit, voltage and current are (a) directly proportional, (b) inversely proportional, (c) not proportional.
6. According to Ohm's Law, what effect will cutting the resistance have on the current?
7. If the voltage stays the same and the resistance is  $\frac{1}{4}$  of its original, what will happen to the current?
8. Using your equation for Ohm's Law, answer the following. Current equals \_\_\_\_\_ divided by \_\_\_\_\_.
9. If the power source is set at 6V and R is 2 ohms, the current = \_\_\_\_\_
10.  $V=5\text{volts}$ ,  $R= 10\text{ ohms}$ ,  $I=$  \_\_\_\_\_.
11. Voltage = \_\_\_\_\_ times \_\_\_\_\_.
12. If the current in the circuit is 7 amps and the resistance is 2 ohms the voltage = \_\_\_\_\_.
13.  $R = 30\text{ ohms}$ ,  $I = 3\text{A}$ ,  $V=$  \_\_\_\_\_
14. Resistance= \_\_\_\_\_ divided by \_\_\_\_\_.

NAME: \_\_\_\_\_ DATE: \_\_\_\_\_

15. If the power source is 12 V and the flow of electrons is 3A, what is the resistance?

16.  $V = 6V$ ,  $I = 18A$ ,  $R =$  \_\_\_\_\_

17. Draw the symbol for a DC power source (battery):

18. Draw the symbol for an AC power source (wall outlet):

19. Draw the symbol for a resistor and explain its effect on a circuit:

20. Draw the symbol for an open switch and explain its effect on a circuit:







21. Draw the symbol for a closed switch and explain its effect on a circuit:

22. Draw the symbol for a capacitor and explain its effect on a circuit:

23. Draw the symbol for an inductor and explain its effect on a circuit:

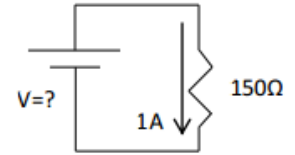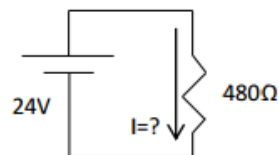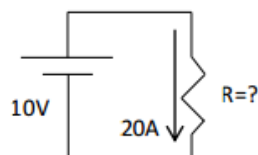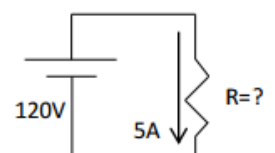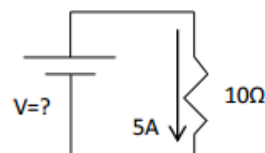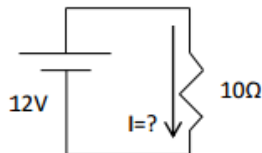24-29:

Solve for the unknown in each of these circuits



NAME: \_\_\_\_\_ DATE: \_\_\_\_\_